

Self Project

Output Voltage Regulation of Buck Converter using Type-2 Compensator

Name: Vikas Pal

July, 2025

Roll No: 244102114

► Objective:

The objective of this experiment is to design a Type-2 compensator for a buck converter to regulate its output voltage.

► Parameters:

Parameter	Value
Input Voltage	24
Inductor	$50\mu\text{H}$
Capacitor	$100\mu\text{F}$
Load resistance	2Ω
Switching frequency	100kHz
Desired gain crossover frequency of compensated system	90 to 120 degrees

► Compensator Design (K factor Method):

For type-2 compensator we have the Transfer function given by

$$G_{C2} = G_{MB} \frac{\left(1 + \frac{\omega_z}{s}\right)}{\left(1 + \frac{s}{\omega_p}\right)} \cdot s \quad (1)$$

where

$$G_{MB} = \frac{1}{\text{Plant gain at } \omega_c} \quad ; \quad \text{Absolute gain}$$

$$\omega_z = \frac{\omega_c}{k}, \quad \omega_p = k\omega_c$$

$$k = \tan\left(45^\circ + \frac{\text{boost}}{2}\right)$$


$$G_{vd} = \frac{-V_{in}}{s^2 LC + \frac{sL}{R} + 1}$$

After substituting the values we got the following Transfer function

$$G_{C2} = \frac{26.54s + 16401}{s^2 + 638s}$$

$$G_{vd} = \frac{24}{5 \times 10^{-9}s^2 + 25e^{-6}s + 1}$$

► Bode Plot:

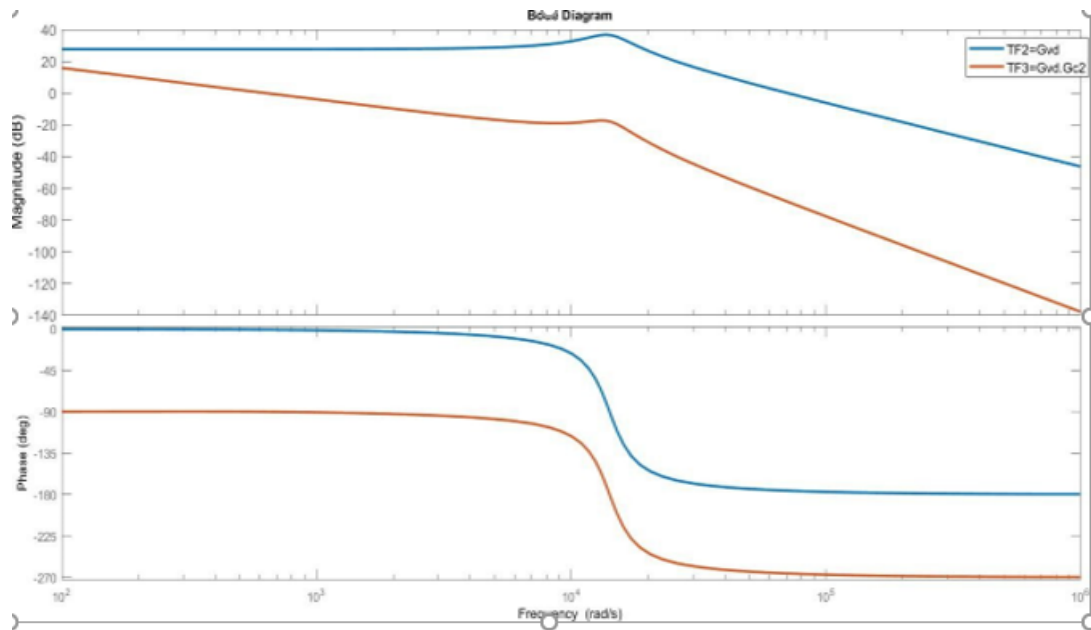

► Stability Margins:


a) G_{vd}

Gain Margin: Inf GM Frequency: Inf
 Phase Margin: 4.2185 PM Frequency: 7.0620×10^4
 Delay Margin: 1.0426×10^{-6} DM Frequency: 7.0620×10^4
 Poles:
 $P_1 = 1.0 \times 10^4 (-0.2500 + j1.3919)$
 $P_2 = 1.0 \times 10^4 (-0.2500 - j1.3919)$

b) G_{C2}


Gain Margin: 7.8542 GM Frequency: 1.4146×10^4
 Phase Margin: 90.0123 PM Frequency: 628.0470
 Delay Margin: 0.0025 DM Frequency: 628.0470
 Poles:
 $P_1 = 0.0000 + 0.0000j$
 $P_2 = -0.2500 + 1.3919j$
 $P_3 = -0.2500 - 1.3919j$
 $P_4 = -0.0638 + 0.0000j$

► MATLAB/SIMULINK SIMULATION:

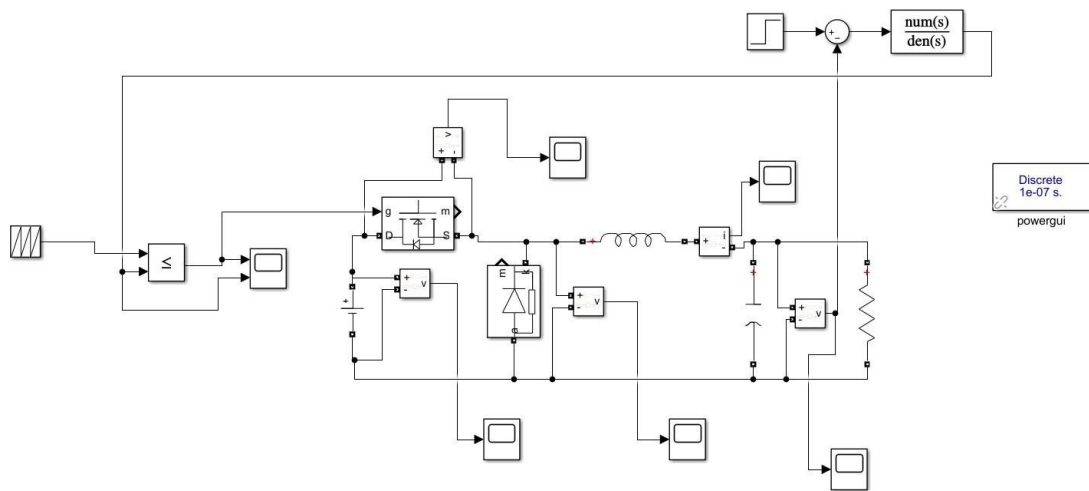


► SIMULATED WAVEFORMS:


(a) input Voltage Waveform

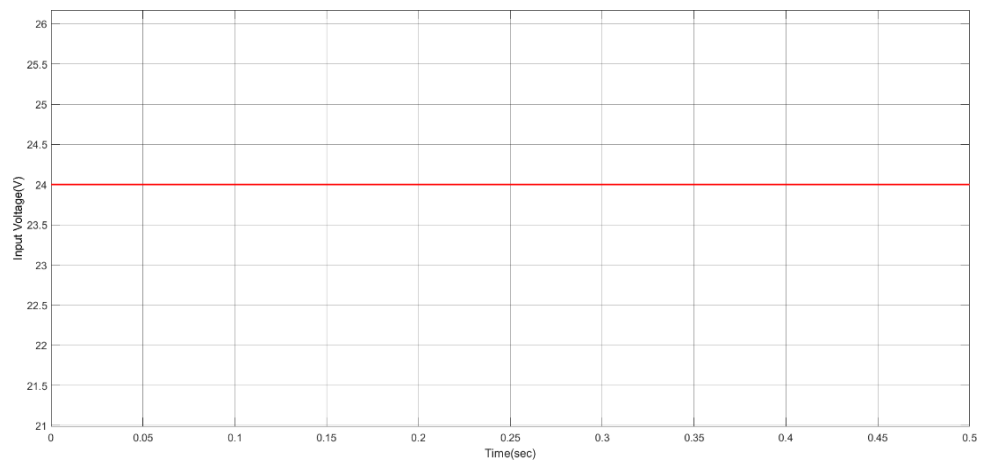


(b) Output Voltage Waveform

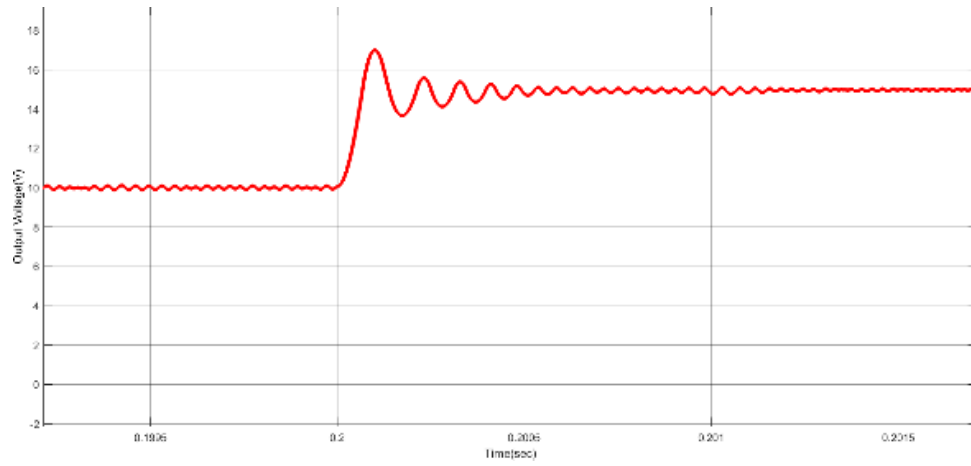


(c) Inductor Current Waveform

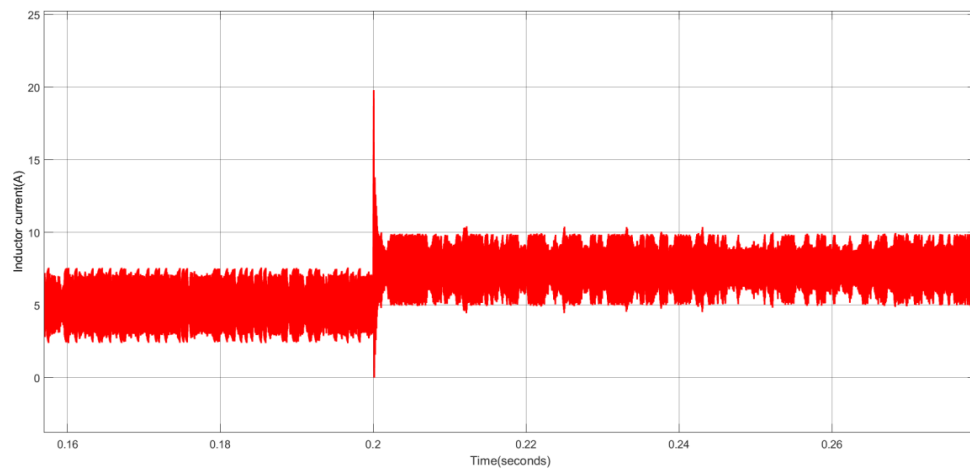

(d) Output Voltage with Compensator

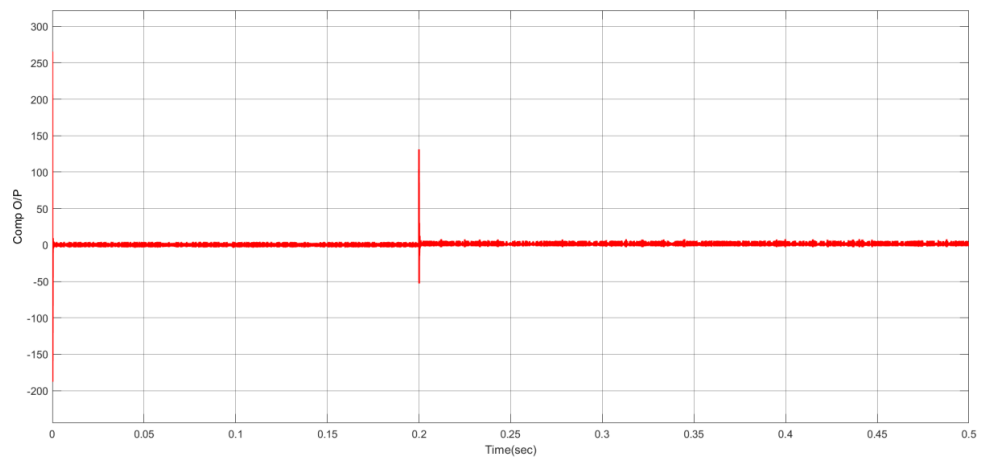

(e) Output Voltage without Compensator

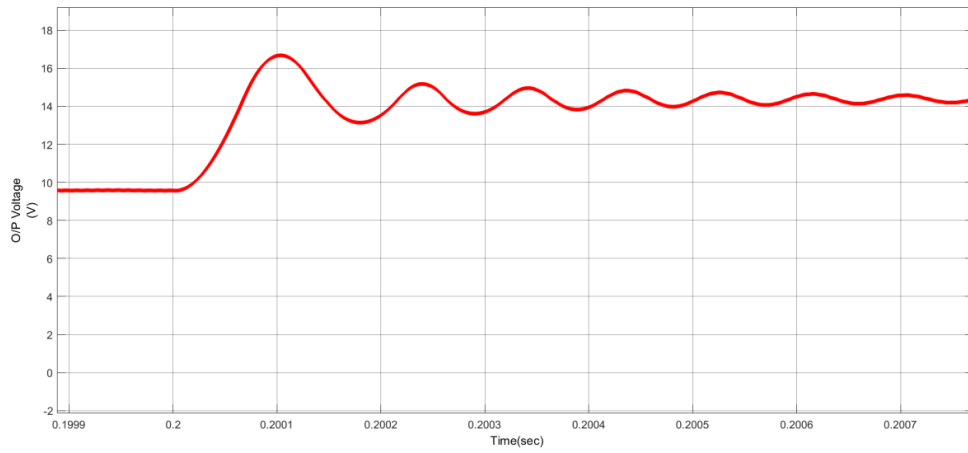

(f) Simulation configuration parameters

Search

Solver

- Data Import/Export
- Math and Data Types
- Diagnosics
- Hardware Implementation
- Model Referencing
- Simulation Target
- Code Generation
- Coverage
- Simscape
- Simscape Multibody

Simulation time

Start time: 0.0 Stop time: 0.5

Solver selection

Type: Fixed-step Solver: ode4 (Runge-Kutta)

▼ Solver details

Fixed-step size (fundamental sample time): 1e-7

Tasking and sample time options

Periodic sample time constraint: Unconstrained

- ☐ Treat each discrete rate as a separate task
- ☐ Allow tasks to execute concurrently on target
- ☐ Automatically handle rate transition for data transfer
- ☐ Higher priority value indicates higher task priority

OK Cancel Help Apply

► Eagle Schematic:

has also been reduced by using the compensator.

Furthermore, the PCB design of the whole system was implemented with the help of **Eagle Software**.